

## Introduction to Digital Systems (21L)

### ELab4: Static Random Access Memory (SRAM)

Please do not edit this report in Teams Files, download it locally on your computer.

Name:

Student Number:

Date:

#### Questions (0.6 pts)

Please answer these questions as shortly as possible (preferably one sentence)

1. What happens to the outputs of set/reset flip-flop (built of NAND gates) when both inputs are in the low state? **(0.1p)**

Ans:

- a. Why? **(0.1p)**

Ans:

2. What is the difference between a D-type latch and a D-type flip-flop? **(0.2p)**

Ans:

3. Please fill all the remaining cells in Table 1. **(0.2p)**

Table 1. Functional description of typical SRAM (basing on Samsung KM62256C SRAM datasheet).

*L – low state, H – high state, X – don't care, High-Z – high impedance state*

$\overline{CS}$	$\overline{OE}$	$\overline{WE}$	Mode	I/O Pin	Power
			Chip deselected		Standby
L	H	H			
				Data in	Active
			Read		

#### Falstad1. SRAM and tri-state buffer (1 pt + 0.7 bonus)

Please fill the underlined spaces.

To write digits 0-9 in SRAM I need \_\_\_\_\_ bits of data.

My Student Number has \_\_\_\_\_ digits, so I need \_\_\_\_\_ address bits to store its digits in SRAM.


The memory content is shown in Table 2.

Table 2. My Student Number and the corresponding digits stored under specified addresses (fill as many columns as you need).

My Student number	SRAM address	0	1	2	3	...	...	...	...	...
	SRAM data									
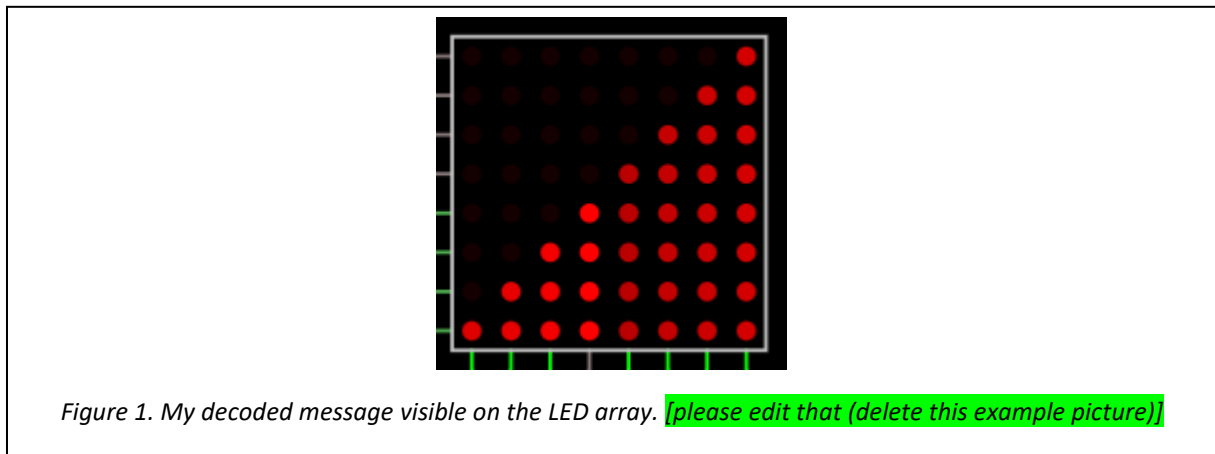
## Falstad2. SRAM (read-only) and multiplex display

In Figure 1 I present my decoded message from task Falstad2.



I declare that this piece of work which is the basis for recognition of achieving learning outcomes in the Introduction to Digital Systems course was completed on my own.