

## Introduction to Digital Systems (21L)

### ELab4: Static Random Access Memory (SRAM)

Name: Yusupov Yuldashbek

Student Number: 317304

Date: 09.05.2021

#### Questions (0.6 pts)

Please answer these questions as shortly as possible (preferably one sentence)

1. What happens to the outputs of set/reset flip-flop (built of NAND gates) when both inputs are in the low state? **(0.1p)**

**Ans:** Both outputs will be in high state.

- a. Why? **(0.1p)**

**Ans:** Because both AND gates will give 0 as outputs and inverted it will be 1, which means high state.

2. What is the difference between a D-type latch and a D-type flip-flop? **(0.2p)**

**Ans:** D-type latch saves data when initially LE signal is on, while D-type flip-flop saves data when CLK signal is on after DATA signal is on

3. Please **fill** all the remaining cells in Table 1. **(0.2p)**

Table 1. Functional description of typical SRAM (basing on Samsung KM62256C SRAM datasheet).

*L – low state, H – high state, X – don't care, High-Z – high impedance state*

$\overline{CS}$	$\overline{OE}$	$\overline{WE}$	Mode	I/O Pin	Power
H	X	X	Chip deselected	High-Z	Standby
L	H	H	Output disabled	High-Z	Active
L	X	L	Write	Data in	Active
L	L	H	Read	Data out	Active

#### Falstad1. SRAM and tri-state buffer (1 pt + 0.7 bonus)

Please **fill** the underlined spaces.

To write digits 0-9 in SRAM I need 4 bits of data.

My Student Number has 6 digits, so I need 3 address bits to store its digits in SRAM.


The memory content is shown in Table 2.

*Table 2. My Student Number and the corresponding digits stored under specified addresses.*

My Student number	SRAM address	0	1	2	3	4	5	...	...	...
317304	SRAM data	4	0	3	7	1	3			
 
### Falstad2. SRAM (read-only) and multiplex display

In Figure 1 I present my decoded message from task Falstad2.



I declare that this piece of work which is the basis for recognition of achieving learning outcomes in the Introduction to Digital Systems course was completed on my own.